Basic transistor use on an Arduino

voltage supply that's different from Arduino motor another motor "flyback" diodes protect the transistors RESET RESET2 D1/ AREF IOREE D3 PWN D5 PWN ULN2803A Arduino Uno АЗ (Rev3) A4/SDA D9 PWN A5/SCL D10 PWM/S D11 PWM/MOS COM - Comn D12/MIS each pin on the left is an input controlling the output straight across from it on the right ICSP2 MISO ICSP2 SC ICSP2 MOS

Arduino ground tied to power supply ground

This circuit uses a ULN2803 transistor, which is actually a single IC (chip) with 8 different transistors in it.

The transistor's job is to act as a switch; the Arduino doesn't need to touch the 6V external power supply shown in this circuit, but can just flip the "switch" on pin 5 to affect the motor on the left, or pin 8 to affect the motor on the right.

A high digital signal from the Arduino will turn the motor on, and a low signal will turn it off. Notice that the motors are always connected to power (they are plugged right into the 6V supply), so what the transistor does in this case is "turn on and off" their connection to ground. It's a funny logic, but it works!

The diodes attached parallel to the motors are there for the protection of the transistors. They are necessary because when power is suddenly shut off to a coil (motors have big coils in them), the coil has a tendency to kick with a high voltage for a brief period. The diodes give that kick somewhere to go so it doesn't damage anything. You don't need diodes like these if you're powering something without a coil, such as an LED strip.

See the other side of this sheet for a sample sketch to try.

Sample Arduino sketch to control the motors. Note that the Arduino has no idea it's got motors attached to it—the sketch is the same as blinking an LED on pin 8 and fading a different LED on pin 5.

```
int motorOne = 5; // shortcut to refer to the motor pin later
int motorTwo = 8;
void setup() {
  pinMode(motorOne, OUTPUT); // we will be writing data to the motor pins
  pinMode(motorTwo, OUTPUT);
}
void loop() {
  // we can "blink" pin 8 (motorOne) by just turning it on for a bit
  digitalWrite(motorOne, HIGH);
  delay(500);
  digitalWrite(motorOne, LOW);
  // we can also fade pin 5 (motorTwo) up and down, because it's a PWM (tilde)
  // pin so it can do analog write in addition to digital write
  // fade from 0 to 255, which is the full range of analogWrite
  for (int i = 0; i < 256; i++) {
    analogWrite(motorTwo, i);
    delay(5);
  }
  // fade back down from 255 to 0
  for (int i = 255; i > 0; i - - ) {
    analogWrite(motorTwo, i);
    delay(5);
  }
}
```